

Conveyor Control with HMI

by
Mike Bullister & Tim Latham
EET275: Intro to PLC
LAB#5
March 16, 2023

Lab Objective:

Control Systems:

Deliverables 2:

- Solenoid = SOLR, Motor = CNVR
- A latch for start and stop (ACT)
- ACT = 1; SOLR (Reset)
- ACT = 1; 3.75s On Delay Timer then CNVR (Set)
- CNVR = 1; 3.25s On Delay Timer then SOLR (Set)
- SOLR = 1; 10s On Delay Time then CNVR (Reset)

Deliverables 3:

- Green Pilot Light = GL and Red Pilot Light = RL
- PROX = Proximity Sensor
- ACT = 1; GL (Set) and RL (Reset)
- ACT = 0; RL (Set) and GL (Reset)
- PROX = 1; INSP (Set)
- PROX = 1 for 3s; Pass (Set) and INSP (Reset)
- Pass = 1; CNVR (Set) Delay Timer On for 5s CNVR (Reset)
- CNVR = 0; Pass (Reset)
- ACT = 0 OR INSP = 1; Fail (Set)
- INSP = 0; Fail (Reset)

Lab Details:


To begin the lab we used the same ladder logic diagram as the previous lab. To begin we divided and conquered with one of us beginning Deliverable 1 and the other finishing Deliverable 2. The first deliverable is the process wiring, which was achieved using the sensor as the only input that needed wired. The outputs used were 02 and 03 for the conveyor motor and the solenoid respectively. After wiring and making sure the ethernet connection was good, we created our HMI.

For Deliverable 2 we used our ladder logic diagram from lab 4 and just implemented our HMI into our ladder logic diagram instead of the start push button, stop pushbutton, and pilot lights. After creating our display with the pilot lights and buttons we declared them to our addresses in our PLC. For Deliverables 3 we were unable to attempt this step due to sickness.

| Name | Address | Input/Output | Device |
|-------------|----------------|---------------------|--------------------|
| STA | IO_EM_D1_00 | Input | Normally Open PB |
| STO | IO_EM_D1_01 | Input | Normally Closed PB |
| PROX | IO_EM_D1_02 | Input | Sensor |
| SOLR | IO_EM_DO_03 | Output | Solenoid |
| CNVR | IO_EM_DO_02 | Output | Motor |
| GL | IO_EM_DO_04 | Output | Green Pilot Light |
| RL | IO_EM_DO_05 | Output | Red Pilot Light |

| Local Variables | |
|------------------------|------------------|
| Name | Data Type |
| ACT | BOOL |
| INSP | BOOL |
| Pass | BOOL |
| Fail | BOOL |

System Schematic:

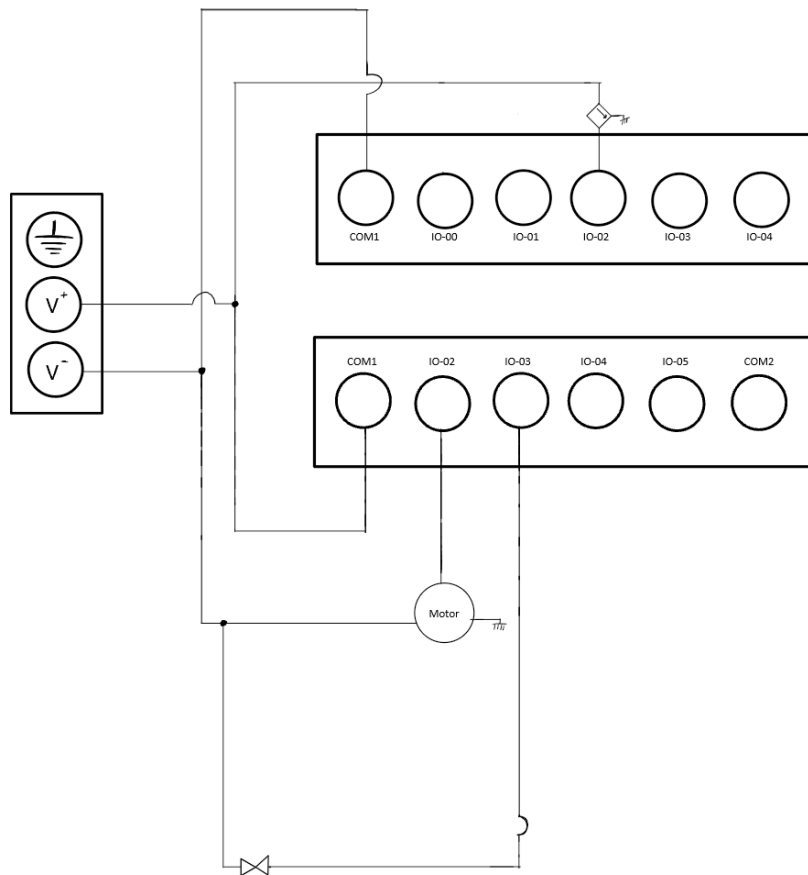

Conclusion:

The purpose of this lab was to learn more about using HMI and the benefits that come with it. Some benefits were less wiring and could be set up and tested away from the PLC. In future labs we can use HMI to test our Ladder Logic Diagram before the lab to test different ideas to save time.